
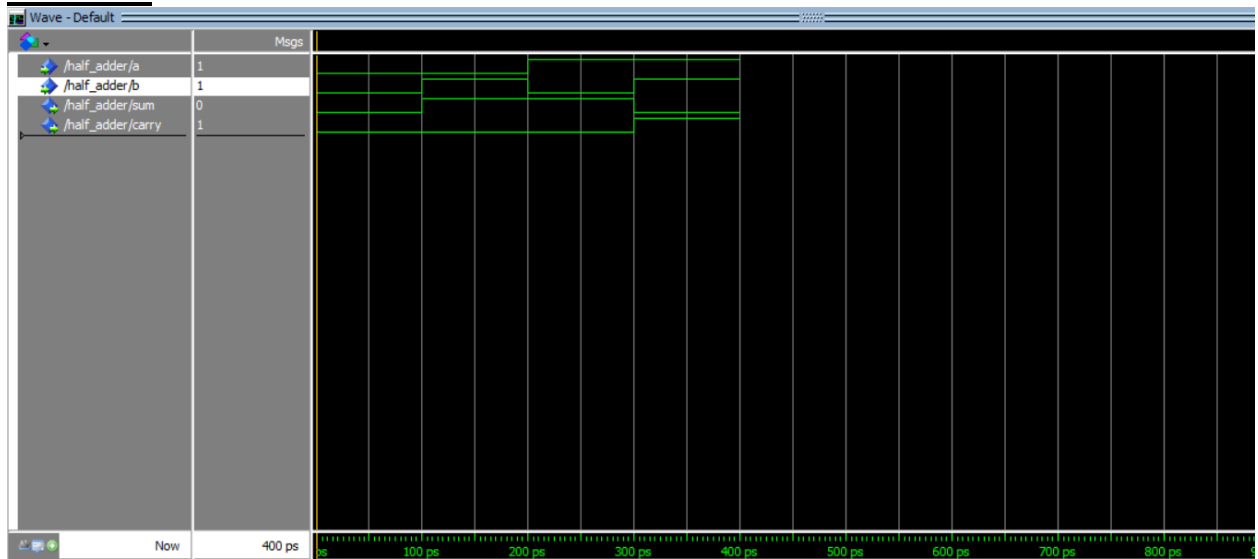


## OUTPUT:

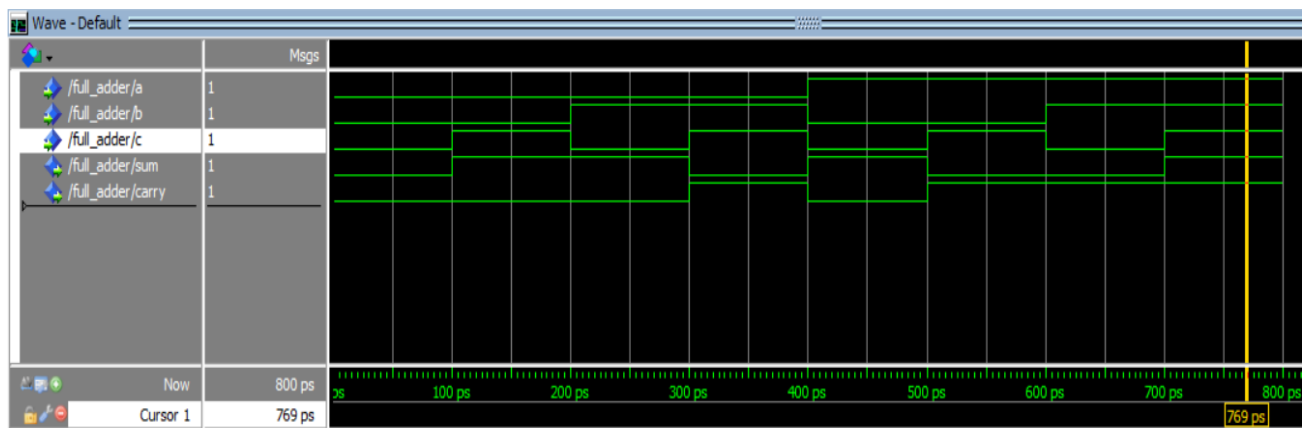

**Fig: Waveform of Half Adder**

## **OUTPUT:**



**Fig: Waveform of Full Adder**

## OUTPUT:


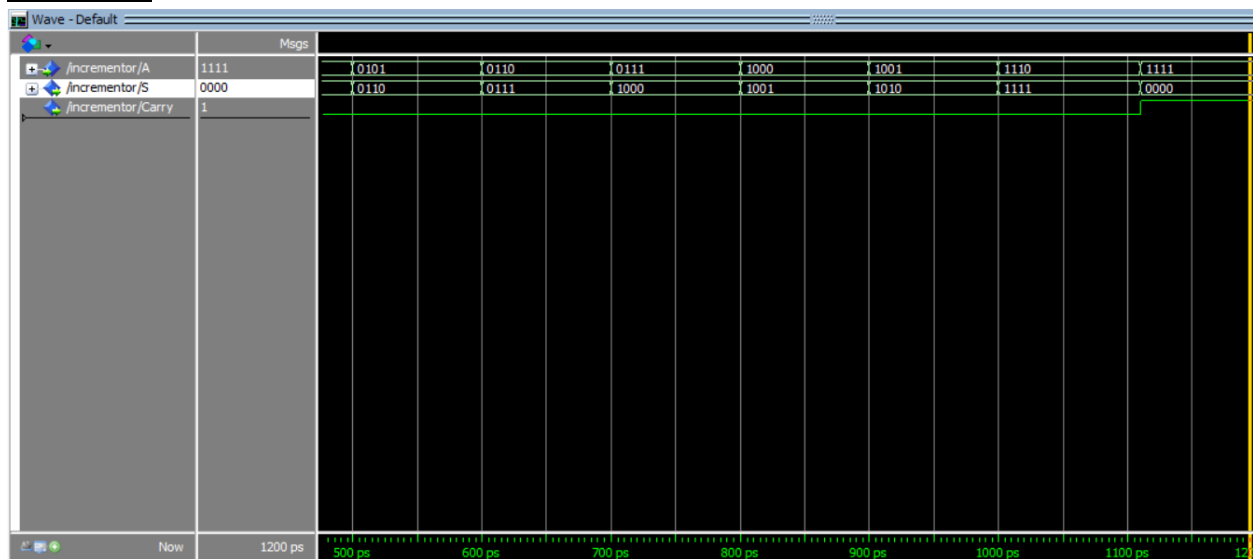


Fig: Waveform of Incrementor

## OUTPUT:

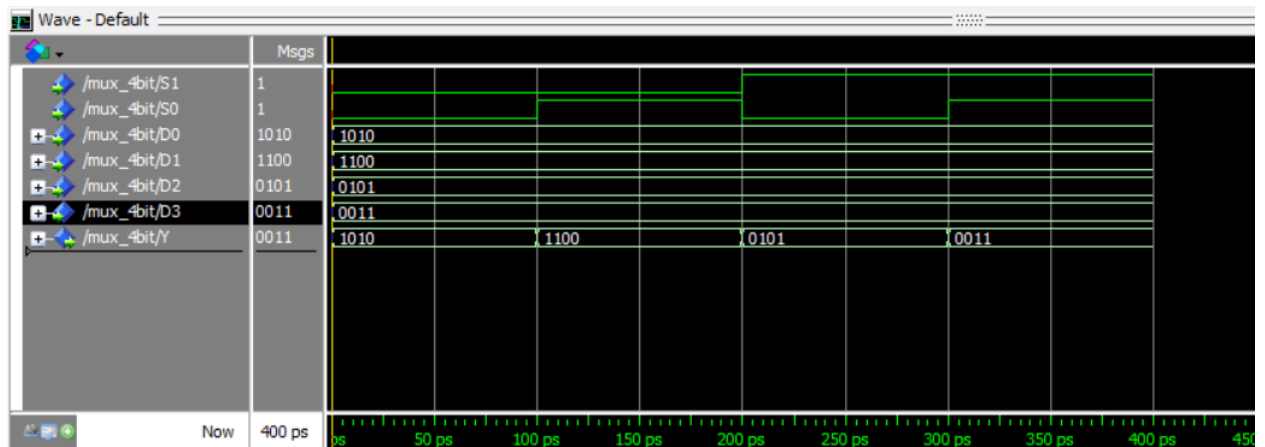

**Fig: Waveform of Multiplexer**

## OUTPUT:



Fig: Waveform of Demultiplexer

## OUTPUT:


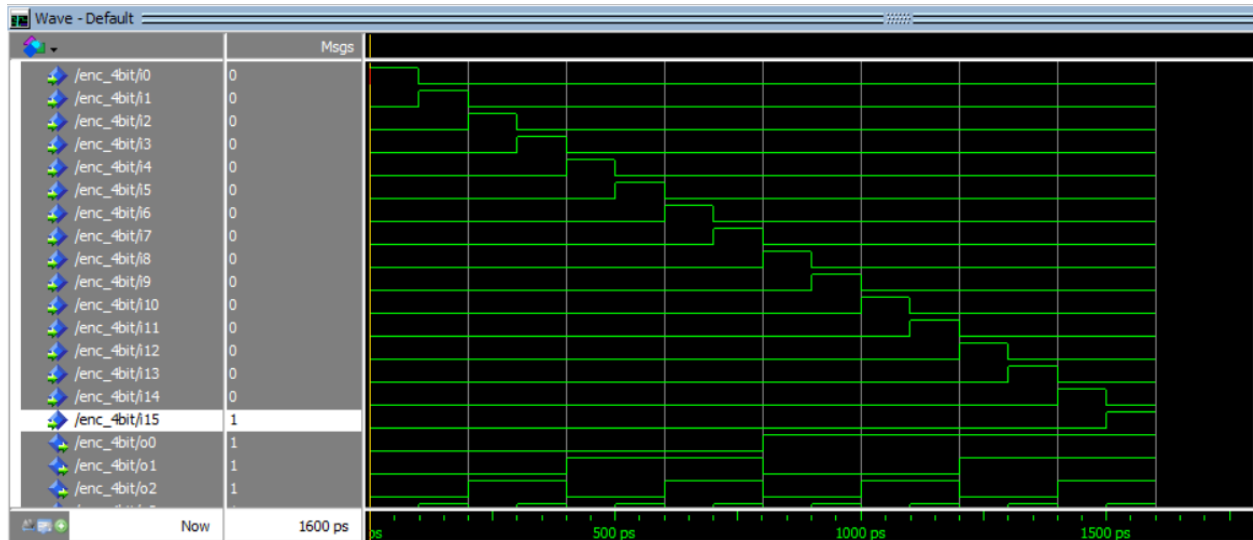


Fig: Waveform of 4-bit Encoder

## OUTPUT:

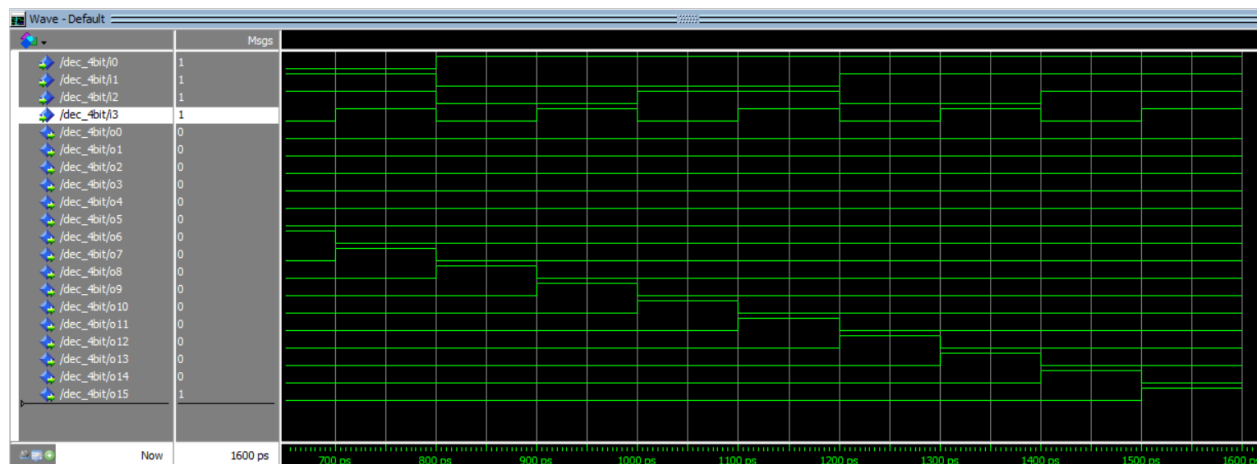

**Fig: Waveform of 4-bit Decoder**